 


Reg. No.: 21BCE1846


Name :

VIT[®]Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)

Continuous Assessment Test II – October 2022

Programme	: B.Tech (CSE, CSE(AIR), CSE(CPS), CSE(AI&ML))	Semester	: FS 2022-23
Course	: Digital System Design	Code	: BECE102L
		Class Nbr	: CH2022231001853
Faculty	: Dr.E.MANIKANDAN	Slot	: E1+TE1
Time	: 90 Minutes	Max. Marks	: 50

Answer ALL the questions

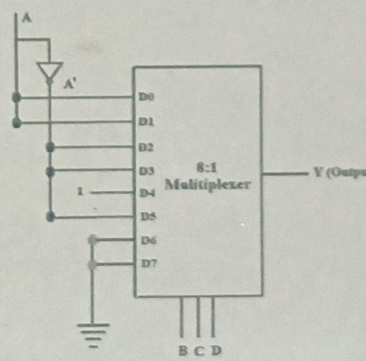Q. No.	Sub-division	Question Text	Marks
1.		<p>Determine the Boolean function implemented in Fig 1 and implement the same Boolean function using suitable Demultiplexer.</p>  <p style="text-align: center;">Figure 1</p>	[5+3]
2.		<p>Determine whether the given function is an even or odd parity generator and write the Verilog code for the same along with the test bench</p> $f(a, b, c) = ab'c' + a'b'c + a'bc' + abc$	[2 + 5]
3.		Use an appropriate algorithm to determine the product of $(-11)_{10} \times (8)_{10}$ and neatly tabulate each cycle.	[10]
4.		Write a Verilog code to subtract two numbers $A = 4'b0101$ and $B = 4'd2$ using adder instantiations.	[10]
5.		In Cheran express, between Coimbatore and Chennai we have only 6 tatkal tickets available under second AC category. Construct a digital circuit using T flip flop which intimates the Railway employee (who books the ticket in the railway station) when the seats are full, by an output signal.	[15]
Total Marks			[50]

⇔⇔⇔

2, 3, 4, 5, 6, 9, 12

1.16